### TWO BIT HALF SUBTRACTOR

#### **EXP.NO: 22**

# AIM:

To design and implement the two bit half subtractor using Logisim simulator.

### PROCEDURE:


- 1) Pick and place the necessary gates.
- 2) Insert 2 inputs into the canvas.
- 3) Connect the inputs to the OR gate, AND gate and NOT gate.
- 4) Insert2 outputs into the canvas.
- Make the connections using the connecting wires.
- 6) Verify the truth table.

#### TRUTH TABLE:

Inputs		Outputs	
Α	В	Diff	Borrow
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

Diff=A'B+AB' Borrow = A'B

# OUTPUT:

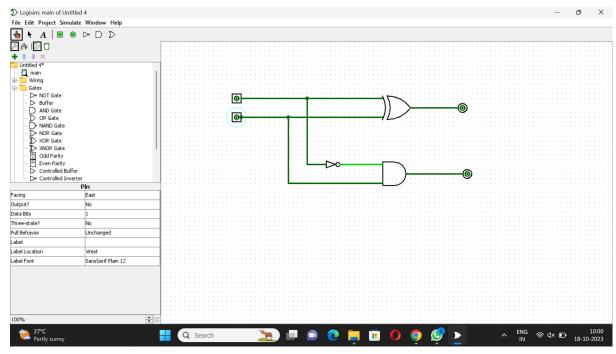

**RESULT:** Thus 2-bit half subtractor has been designed and implemented successfully using logisim simulator